

UNIVERSITY OF TEXAS AT DALLAS

800 W Campbell Rd, Richardson, TX 75080, USA



VLSI DESIGN (EECT 6325)

Project Done On:

INVERTER DESIGN, LAYOUT AND SIMULATION

Team Members:

GOKUL SAI RAGHUNATH	GXR200021
ABHISHEK MAHESH KUMAR	AXM200255
SOMA RAJ KUMAR	RXS190135

Obtained Result:

1.	ENERGY (E)	-1.076e - 11
2.	DELAY (D)	1.104e - 10
3.	EDP	1.188e - 23
4.	AREA	W = 0.649 um & H = 5.539 um A = W*H = 3.594 pm ²


ACKNOWLEDGEMENT

We are grateful to Professor CARL SECHEN for providing us an opportunity to explore and conduct projects based on VLSI Design.


We also take this opportunity to express our gratitude to MR VAIBHAV KUMARSWAMY SALIMATH for his guidance in conducting the project.

INTRODUCTION

 An inverter circuit outputs a voltage representing the opposite logic-level to its input. Its main function is to invert the input signal applied. If the applied input is low then the output becomes high and vice versa. Inverters can be constructed using a single NMOS transistor or a single PMOS transistor. It is called as CMOS inverter as it has both NMOS and PMOS




INVERTER LAYOUT

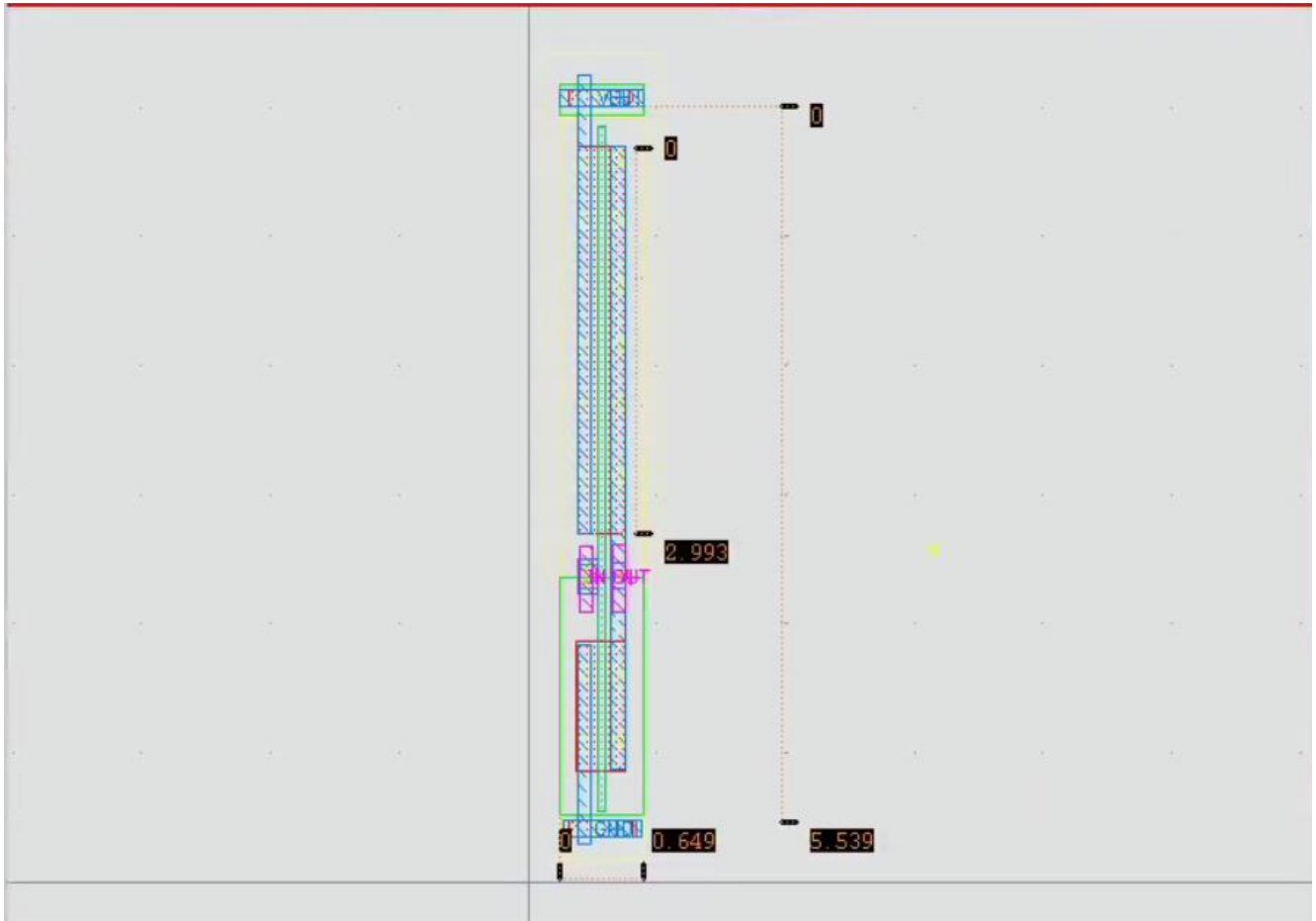

The MOS inverter we designed has a gate width of 0.06 μm , the width of pMOS being 3 μm and the width being 1 μm . Here we have maintained the pMOS to nMOS width ratio as 3:1.

The distance between the top and bottom M1 metal layer is 5.539 μm and the width is 0.649 μm . The total area is 3.59 μm^2 .

INVERTER SCHEMATIC

 

DESIGN RULE CHECK OUTPUT

Calibre - RVE v2013.2.18.13 : inv.drc.results

File View Highlight Tools Window Setup Help

Show All inv, 0 Results (in 0 of 2078 Checks)

Check / Cell	Results
✓ Check GRS2	0
✓ Check GRS6	0
✓ Check GRB_BF01	0
✓ Check GRSRB_BF01	0
✓ Check GRB_BF02	0
✓ Check GRB_BF03	0
✓ Check GRB_BF04	0
✓ Check GRB_BH01	0
✓ Check GRB_BH02	0
✓ Check GRSRB_BH02	0
✓ Check GRB_BH03	0
✓ Check GRB_BH04	0
✓ Check GRSRB_BH04	0
✓ Check GRB_DE01	0

Rule File Pathname: /home/eng/g/gxr200021/cad/gf65/inv_DRC/_Calibre_DRC_rules_
Rule File Title: YI-DM00054.09 - YI-RT00052.12
Shapes with acute angles are prohibited (Except for PROTECT Layer)

Check GRS2

The DESIGN RULE CHECK was successful with zero errors.

Calibre - RVE v2013.2-18.13 : svdb inv

File View Highlight Tools Window Setup

Search

Navigator

Comparison Results

Layout Cell / Type	Source Cell	Nets	Instances	Ports
inv	inv	4L, 4S	1L, 1S	4L, 4S

Results

- Extraction Results
- Comparison Results
- Parasitics

ERC

- ERC Results
- ERC Summary

Reports

- Extraction Report
- LVS Report

Rules

- Rules File

View

- Info
- Finder
- Schematics

Setup

- Options

Cell inv Summary (Clean)

CELL COMPARISON RESULTS (TOP LEVEL)

```

      #
      #
    #  #
    #  #
    #

#####
#      #
#  CORRECT  #
#      #
#####


```

LAYOUT CELL NAME: inv
SOURCE CELL NAME: inv

INITIAL NUMBERS OF OBJECTS

The LAYOUT VS SCHEMETIC test was also successful with zero warnings.

CREATION OF PEX FILE FOR H-SPICE

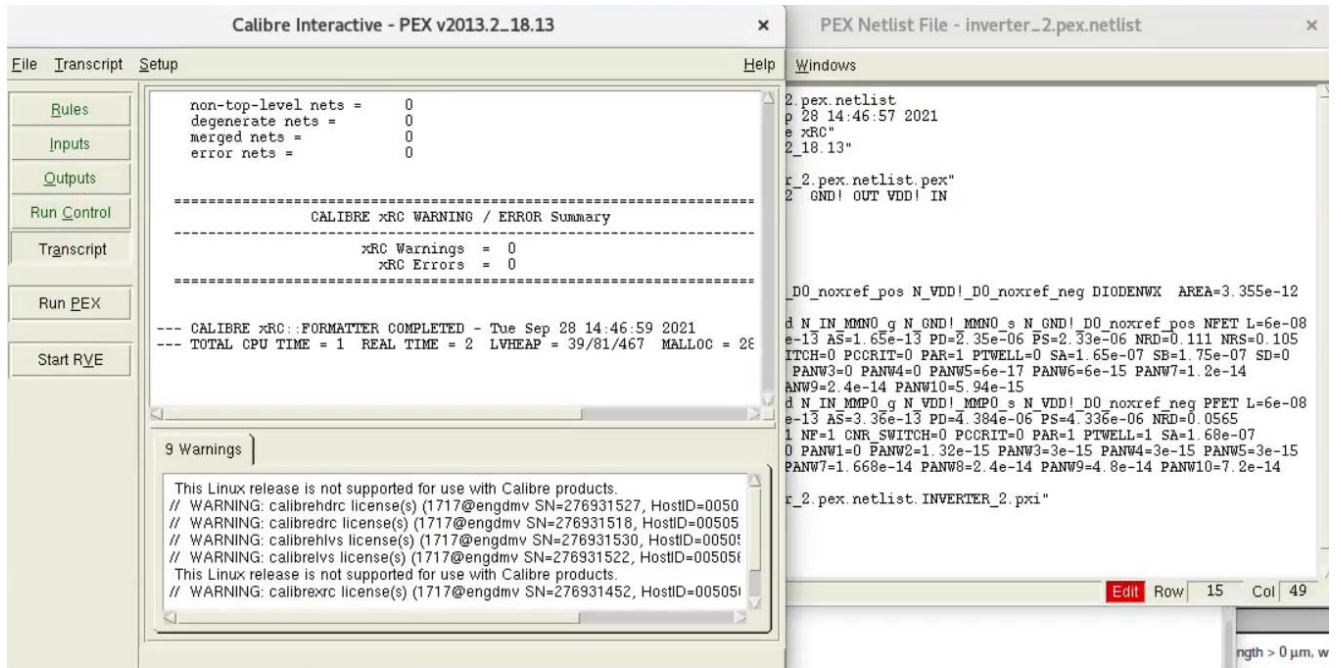

SPICE TEST SETUP FILE

\$example HSPICE setup file

\$transistor model

.include "/proj/cad/library/mosis/GF65_LPe/cmos10lpe_CDS_oa_dl064_11_20160415/models/YI-SM00030/Hspice/models/design.inc"

.include "inv.pex.netlist"

.option post runlvl=5

xi GND! OUT VDD! IN inv

vdd VDD! GND! 1.2v

vin IN GND! pwl(0ns 1.2v 1ns 1.2v 1.0833ns 0v 6ns 0v 6.0833ns 1.2v 12.00ns 1.2v)

cout OUT GND! 70f

\$transient analysis

.tr 100ps 12ns

\$example of parameter sweep, replace numeric value W of pfet with WP in invlvs.sp

\$.tr 100ps 12ns sweep WP 1u 9u 0.5u

.measure tran trise trig v(IN) val=0.6v fall=1 targ v(OUT) val=0.6v rise=1 \$measure tlh at 0.6v

.measure tran tfall trig v(IN) val=0.6v rise=1 targ v(OUT) val=0.6v fall=1 \$measure tpl at 0.6v

.measure tavg param = '(trise+tfall)/2' \$calculate average delay

.measure tdiff param='abs(trise-tfall)' \$calculate delay difference

.measure delay param='max(trise,tfall)' \$calculate worst case delay

\$ method 1

.measure tran iavg avg i(vdd) from=0 to=10n \$average current in one clock cycle




.measure energy param='1.2*iavg*10n' \$calculate energy in one clock cycle

.measure edp1 param='abs(delay*energy)'

.end

EDP MINIMIZATION

The EDP of the first design was $1.197e - 23$ with pMOS to nMOS ratio of 3:1 and the area being 5.9384 pm^2 . Our current design was able to achieve EDP of $1.188e - 23$ with the same pMOS and nMOS ratio with the area of 3.594 pm^2 . This reduction in EDP was achieved by reducing the width by 0.355 um (from 1.04 um to 0.649 um) and also height by 0.171 um (from 5.71 um to 5.539 um). By this reduction in height and width resulted in the reduction in overall area, which further minimized the value of EDP.

 inv.mt0 ~/cad/spice/SP2			
Open ▾		Save	 
\$DATA1 SOURCE='HSPICE' VERSION='L-2016.06-SP1-2 linux64' PARAM_COUNT=0			
.TITLE '\$example hspice setup file'			
trise	tfall	tavg	tdiff
delay	iavg	energy	edp1
temper	alter#		
8.829e-11	1.104e-10	9.935e-11	2.212e-11
1.104e-10	-8.969e-06	-1.076e-13	1.188e-23
25.0000	1		

HEIGHT AND WIDTH OF nMOS & pMOS

 


Fig. Height of nMos

 


Fig. Height of pMOS


 


Fig. Width

I/O WAVEFORM

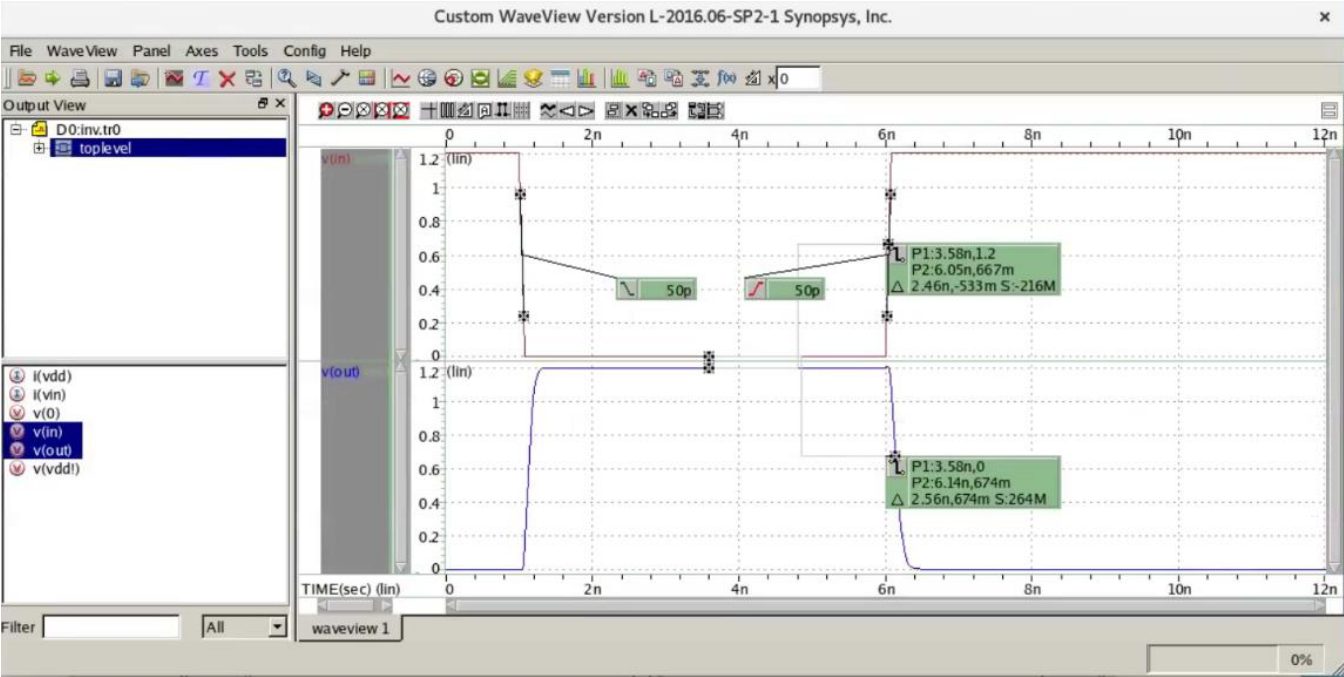

CONCLUSION

The inverter layout and schematic designed through the cadence tool was successful completed without any errors by passing both DRC and LVS test. Our design has also successfully minimized the value of EDP and the result obtained has been plotted on WaveView.